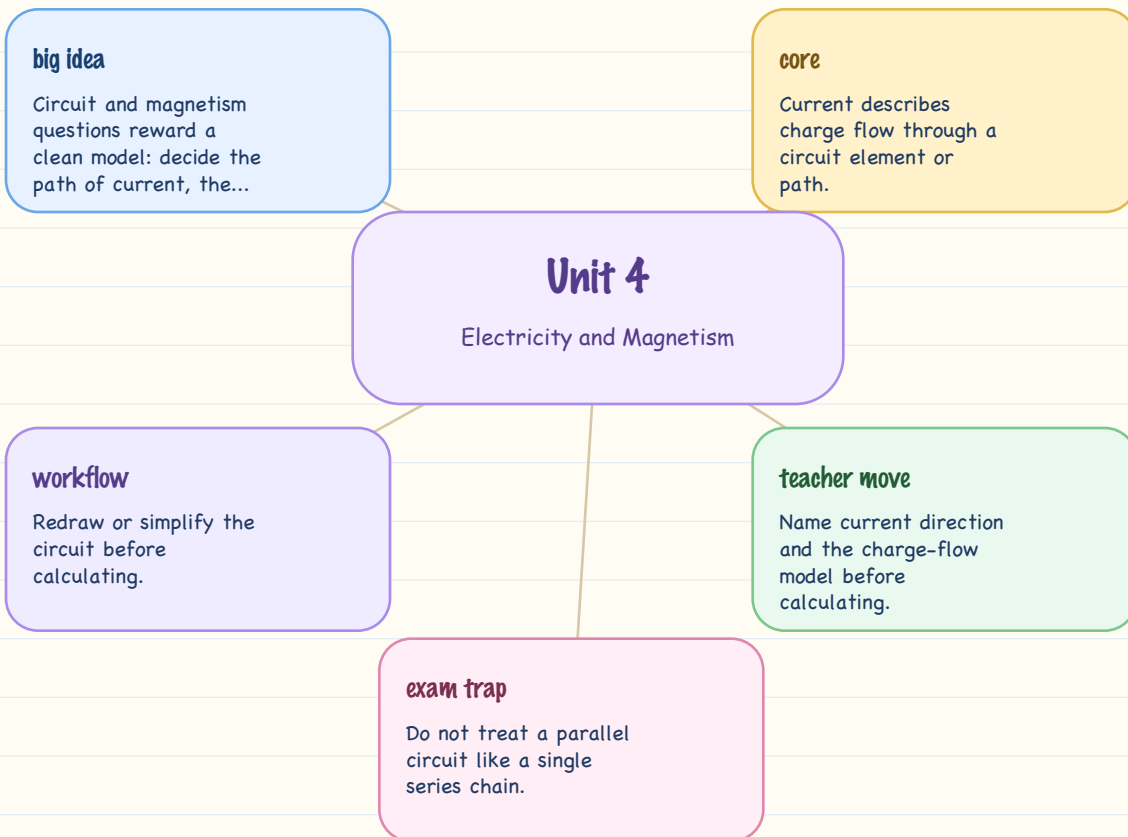


## Unit 4 Visual Notebook


# Electric Circuits, Magnetism, and Ampere Force

### DISTILLED FROM VIDEO

Diagram-first study pages using the same source-locked SPH3U workflows and teacher moves.



# Visual Strategy

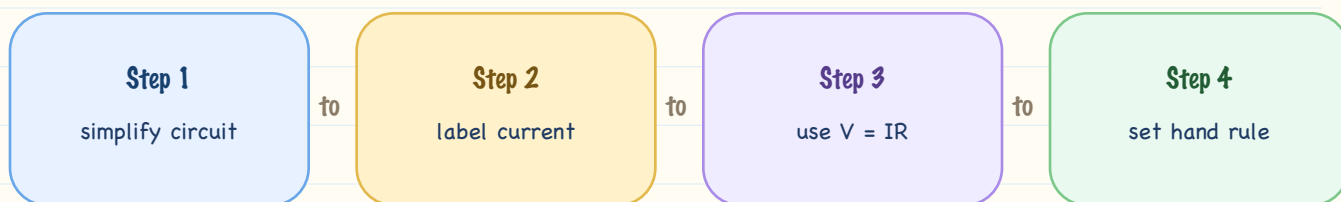

## Use this when stuck

- Redraw or simplify the circuit before calculating.
- Label current direction and potential differences.
- Choose the series, parallel, or mixed-circuit rule that fits the structure.
- For magnetic direction questions, set the hand rule before deciding the result.
- Check the unit: ampere, volt, ohm, tesla, newton, or joule.

## Video teacher tips

- Name current direction and the charge-flow model before calculating.
- Simplify the circuit structure before using formulas.
- Read the graph feature first: slope, area, intercept, or trend.
- Set the right-hand rule carefully before naming a magnetic direction.
- Set directions before assigning signs or writing equations.
- Use parallel-circuit rules only after identifying shared endpoints.

## Example and Recall

### Worked example pattern

One-resistor circuit (Unit 4 distilled pattern: identify current, voltage, and resistance before calculating)

Use the simple circuit relationship  $V = IR$ .

If  $V = 12 \text{ V}$  and  $R = 4 \ \Omega$ , solve for  $I$ .

$I = V/R = 12/4$ .

Attach the unit ampere.

Answer pattern:  $I = 3 \text{ A}$ .

Magnetic direction routine (Unit 4 distilled pattern: use the direction rule before solving motion)

Identify the current direction.

Identify the magnetic-field direction.

Use the hand rule named by the source lesson.

### Quick recall prompts

- Use  $V = IR$  in a one-resistor context.
- Identify whether current or voltage is shared in series or parallel parts.
- Use a direction rule for a current-carrying wire in a magnetic field.